

(a) Hardware: Unpipelined



(b) Pipeline diagram

Measure circuit delays in units of picoseconds (ps) $\rightarrow 10^{-12}$ seconds


limited by the slowest stage

Throughput: maximum rate at which we could operate the system


$$\text{Throughput} = \frac{1 \text{ instruction}}{(20 + 300) \text{ picoseconds}} \cdot \frac{1,000 \text{ picoseconds}}{1 \text{ nanosecond}} \approx 3.12 \text{ GIPS}$$

\rightarrow giga-instructions per sec.

 Latency: The total time required to perform a single instruction from beginning to end.



(a) Hardware: Three-stage pipeline

 


(b) Pipeline diagram

processing a single instruction requires 3 clock-cycle.


Latency = $3 \times 120 = 360$ ps

$$\text{Throughput} = \frac{3 \text{ instructions}}{360 \text{ ps}} \times \frac{1,000 \text{ ps}}{1 \text{ ns}} \approx 8.33 \text{ GIPS}$$

Non-uniform partitioning

 

 (a) Hardware: Three-stage pipeline, nonuniform stage delays



(b) Pipeline diagram

Sum of the delays through all of the stages

remains 300 ps. BUT, the rate at which we can operate the clock is limited by the delay of the slowest stage.

clock cycle: $150 + 20 = 170$ ps

$$\text{throughput} = \frac{1}{170} \times \frac{1,000 \text{ ps}}{1 \text{ ns}} = 5.88 \text{ GIPS}$$

$$\text{latency} = 3 \times 170 = 510 \text{ ps}$$